

PART 1: DIGITAL DESIGN THEORY

Provide your answers here:

1.

AB \ CD	00	01	11	10
00	m_0 1	m_1 1	m_3	m_2
01	m_4	m_5 1	m_7	m_6
11	m_{10}	m_{13} 1	m_{15}	m_{14}
10	m_8	m_9 1	m_{11} 1	m_{12} 1

According to K-map:

$$m_0 + m_1 + m_8 + m_9 = B'C'$$

$$m_1 + m_5 + m_{13} + m_9 = C'D$$

$$m_{13} + m_{15} + m_9 + m_{11} = AD$$

$$m_8 + m_9 + m_{11} + m_{10} = AB'$$

$$\therefore F(A, B, C, D) = AB' + C'D + AD + B'C'$$

$$\text{由 } \overline{A/B} = \overline{(A \cup B)}$$

$$(b) F(A, B, C, D) = (A' + B)' + (C + D')' + (A' + D')' + (B + C)'$$

$$(c) F(A, B, C, D) = [(AB')'(C'D)(AD)'(B'C)']'$$

$$(d) F(A, B, C, D) = A(B' + D) + C'(B' + D) \\ = (A + C')(B' + D)$$

$$(e) F(A, B, C, D) = [(A + C')' + (B' + D)']'$$

$$(f) F(A, B, C, D) = (A'C)'(BD')'$$

2. four-bit parity generator:


A	B	C	D	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

According to the truth-table, we can gain its K-map:

AB \ CD	00	01	11	10
00	m_0 1	m_1	m_3 1	m_2
01	m_4	m_5 1	m_7	m_6 1
11	m_{12} 1	m_{13}	m_{15} 1	m_{14}
10	m_8	m_9 1	m_{11}	m_{10} 1

$$\therefore P = (A \oplus B \oplus C \oplus D)'$$

\therefore the circuit diagram:

 

three-bit parity checker:


A	B	C	P	CP
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0

A	B	C	P	CP
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

like four-bit parity generator:

$$CP = (A \oplus B \oplus C \oplus P)'$$

the circuit diagram:

 

3. the truth table:

x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

the K-map:

A:

yz \ x	00	01	11	10
0	m ₀	m ₁	m ₃	m ₂
1	m ₄	m ₅	m ₇	m ₆

$$A = y + xz$$

B:

yz \ x	00	01	11	10
0	m ₀	m ₁	m ₃	m ₂
1	m ₄	m ₅	m ₇	m ₆


$$B = yz' + xy' + xyz$$

C:

yz \ x	00	01	11	10
0	m ₀	m ₁	m ₃	m ₂
1	m ₄	m ₅	m ₇	m ₆

$$C = x'z + xz'$$

the circuit diagram

 


4. 3-bit x 3-bit

logic formulas:

$$\begin{array}{r}
 B_2 \ B_1 \ B_0 \\
 A_2 \ A_1 \ A_0 \\
 \hline
 A_0B_2 \ A_0B_1 \ A_0B_0 \\
 A_1B_2 \ A_1B_1 \ A_1B_0 \\
 A_2B_2 \ A_2B_1 \ A_2B_0 \\
 \hline
 C_5 \ C_4 \ C_3 \ C_2 \ C_1 \ C_0
 \end{array}$$

the circuit diagram:

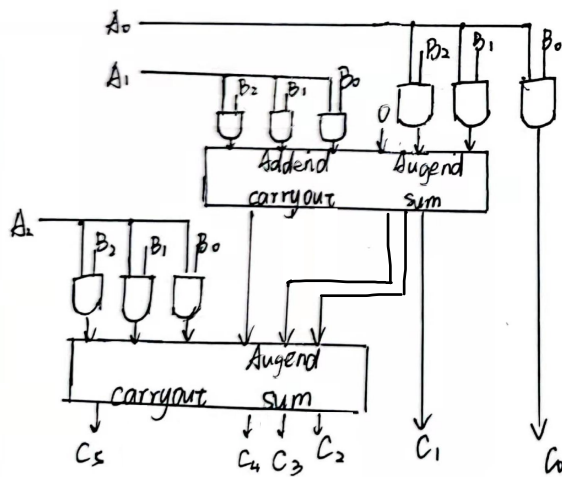

description:

from the logic formula:

we know

C_0 just needs AND, doesn't need an adder and to get $C_5 \ C_4 \ C_3 \ C_2 \ C_1$, we need two adders

one is for $A_0B_2 \ A_0B_1$ and $A_1B_2 \ A_1B_1 \ A_1B_0$ another is for $A_2B_2 \ A_2B_1 \ A_2B_0$ and the carryout from the first adder.

then, we can get the circuit diagram

5. (a) $F(A, B, C, D) = \Sigma(1, 3, 5, 8, 10, 14)$

1 should be connected to input ports $D_1, D_3, D_5, D_8, D_{10}, D_{14}$

0 should be connected to input ports $D_0, D_2, D_4, D_6, D_7, D_9, D_{11}, D_{12}, D_{13}, D_{15}$

(b) $F(A, B, C, D) = \Pi(4, 7, 11)$

$$= \Sigma(0, 1, 2, 3, 5, 6, 8, 9, 10, 12, 13, 14, 15)$$

1 should be connected to input ports $D_0, D_1, D_2, D_3, D_5, D_6, D_8, D_9, D_{10}, D_{12}, D_{13}, D_{14}, D_{15}$


0 should be connected to input ports D_4, D_7, D_{11}



b.

X	Y	Bin	Bout	Diff
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

∴ the circuit diagram

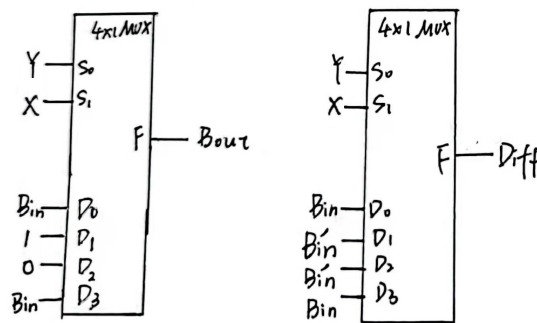

PART 2: DIGITAL DESIGN LAB (TASK1)

DESIGN

Describe the design of your system by providing the following information:

- Verilog design (provide the Verilog code)

```
module decoder_74138(A,B,C,G1,G2A_n,G2B_n,Y_n);
```

```
input A,B,C,G1,G2A_n,G2B_n;
```

```
output reg[7:0] Y_n;
```

```
always@(*) begin
```

```
if(G1==1 && G2A_n==0 && G2B_n==0)
```

```
begin
```

```
case({C,B,A})
```

```
3'b000: Y_n= 8'b1111_1110;
```

```
3'b001: Y_n= 8'b1111_1101;
```