



## **DIGITAL DESIGN**

## **ASSIGNMENT REPORT**

**ASSIGNMENT ID: 12010423**


**Student Name: 张嘉浩**

**Student ID: 12010423**

## PART 1: DIGITAL DESIGN THEORY

Provide your answers here:

张嘉浩 12010423.

 

(a) AND-OR:  $F = AB' + AD + C'D + B'C'$

(b) NOR-OR:  $F = (A'+B)' + (A'+D)' + (C+D)' + (B+C)'$

(c) NAND-NAND:  $F = ((AB')'(AD)'(C'D)'(B'C')')'$

(d) OR-AND:  $F' = A'C + BD'$   
 $F = (A+C')(B'+D)$

(e) NOR-NOR:  $F = ((A+C')' + (B'+D)')'$

(f) NAND-AND:  $F = (A'C)'(BD)'$   ~~$F = (AC)'$~~





2. 4 bit parity generator:

① Truth-table.

A	B	C	D	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

3 bit parity checker.  
② Truth-table.

A	B	C	P	R.
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1



## 2. ② Simplification .


Both can be ~~sim~~simplified to the same logic equation (same Kmap).

CD \ AB		C			
		00	01	11	10
A	00	1	0	1	0
	01	0	1	0	1
	11	1	0	1	0
	10	0	1		1

thus both equation are:

$$F = (A \oplus B \oplus C \oplus D)'$$

 ③ Both shared the same logic diagram as below



3.

input			output		
X	Y	Z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

A:

x \ yz	y			
	00	01	11	10
0	0	0	1	1
1	0	1	1	1

z

$$A = xz + y$$

B:

x \ yz	y			
	00	01	11	10
0	1	1	0	0
1	1	0	1	0

z

$$B = x'y' + (x \oplus z)'$$

C:


x \ yz	y			
	00	01	11	10
0	0	1	1	0
1	1	0	0	1

z

$$C = x'z + xz'$$




3. Circuit diagram.

 

4.

		$A_2$	$A_1$	$A_0$	
$\times$		$B_2$	$B_1$	$B_0$	
		$A_2B_0$	$A_1B_0$	$A_0B_0$	
		$A_2B_1$	$A_1B_1$	$A_0B_1$	
		$A_2B_2$	$A_1B_2$	$A_0B_2$	
$C_5$	$C_4$	$C_3$	$C_2$	$C_1$	$C_0$

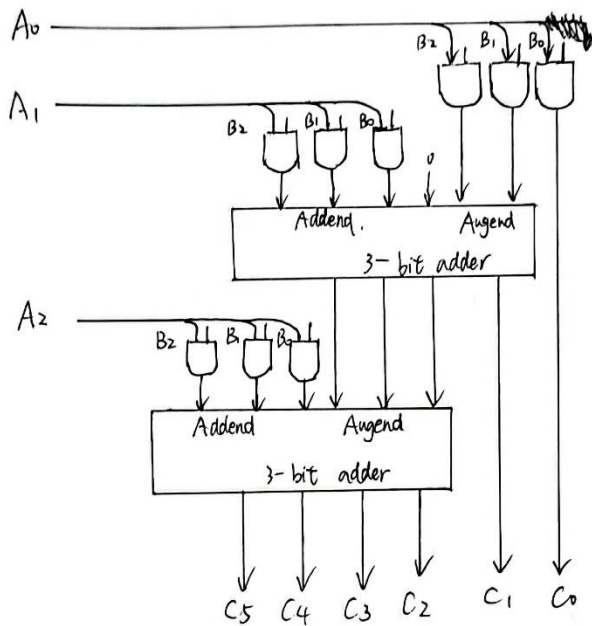$C_0 = A_0B_0$   
 $C_1 = A_1B_0 + A_0B_1$   
 $C_2 = A_2B_0 + A_1B_1 + A_0B_2$   
 $C_3 = A_2B_1 + A_1B_2$   
 $C_4 = A_2B_2$





$$5. (a) F(A, B, C, D) = \sum (1, 3, 5, 8, 10, 14)$$

$$= 0 \times A'B'C'D' + 1 \times A'B'C'D + 0 \times A'B'CD' + 1 \times A'B'CD + 0 \times A'BC'D' + 1 \times A'BC'D + 0 \times A'BCD' + 0 \times A'BCD + 1 \times AB'C'D' + 0 \times AB'C'D + 1 \times AB'CD' + 0 \times AB'CD + 0 \times ABC'D' + 0 \times ABC'D + 1 \times ABCD' + 0 \times ABCD$$

$$= \sum_{i=0}^{15} D_i m_i$$

$$= m_0 \times 0 + m_1 \times 1 + m_2 \times 0 + m_3 \times 1 + m_4 \times 0 + m_5 \times 1 + m_6 \times 0 + m_7 \times 0 + m_8 \times 1 + m_9 \times 0 + m_{10} \times 1 + m_{11} \times 0 + m_{12} \times 0 + m_{13} \times 0 + m_{14} \times 1 + m_{15} \times 0.$$

$$(b) F(A, B, C, D) = \prod (4, 7, 11)$$

$$= \sum (0, 1, 2, 3, 5, 6, 8, 9, 10, 12, 13, 14, 15)$$

$$= 1 \times A'B'C'D' + 1 \times A'B'C'D + 1 \times A'B'CD' + 1 \times A'B'CD + 0 \times A'BC'D' + 1 \times A'BC'D + 1 \times A'BCD' + 0 \times A'BCD + 1 \times AB'C'D' + 1 \times AB'C'D + 1 \times AB'CD' + 0 \times AB'CD + 1 \times ABC'D' + 1 \times ABC'D + 1 \times ABCD' + 1 \times ABCD$$



$$= \sum_{i=0}^{15} D_i m_i$$

$$= m_0 \times 1 + m_1 \times 1 + m_2 \times 1 + m_3 \times 1 + m_4 \times 0 + m_5 \times 1 + m_6 \times 1 + m_7 \times 0 + m_8 \times 1 + m_9 \times 1 + m_{10} \times 1 + m_{11} \times 0 + m_{12} \times 1 + m_{13} \times 1 + m_{14} \times 1 + m_{15} \times 1.$$



6.

X	Y	Bin	Diff	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

  

Simplification:


X \ Y Bin	00	01	11	10
0	0	1	0	1
1	1	0	1	0

(Kmap for Diff)

thus  $\text{Diff} = X \oplus Y \oplus \text{Bin}$

X \ Y Bin	00	01	11	10
0	0	1	1	1
1	0	0	1	0

 thus  $\text{Bout} = X' \text{Bin} + X' Y + Y \text{Bin}$



## PART 2: DIGITAL DESIGN LAB (TASK1)

### DESIGN

**(This part is always REQUIRED)**

Describe the design of your system by providing the following information:

- Verilog design (provide the Verilog code)

```
1  `timescale 1ns / 1ps
2
3  module decoder_74138 (A,B,C,G1, G2a, G2b, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
4      input A, B, C;
5      input G1, G2a, G2b;
6      output reg Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7;
7
8      always @ (*)
9      begin
10         if (G1 & G2a & G2b)
11         begin
12             case ({A, B, C})
13                 3'b000: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_0001;
14                 3'b001: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_0010;
15                 3'b010: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_0100;
16                 3'b011: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_1000;
17                 3'b100: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0001_0000;
18                 3'b101: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0010_0000;
19                 3'b110: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0100_0000;
20                 3'b111: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b1000_0000;
21                 default: {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_0000;
22             endcase
23         end
24         else
25         begin
26             {Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7} = 8'b0000_0000;
27         end
28     end
29 endmodule
```

•

```

1  `timescale 1ns / 1ps
2
3  module decoder_4_16(A, B, C, D, G1, G2a, G2b,
4      Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7,
5      Y8, Y9, Y10, Y11, Y12, Y13, Y14, Y15);
6      input A, B, C, D, G1, G2a, G2b;
7      output Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7, Y8, Y9, Y10, Y11, Y12, Y13, Y14, Y15;
8      decoder_74138 d1(A, B, C, D, G1, G2a, G2b, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
9      decoder_74138 d2(A, B, ~C, D, G1, G2a, G2b, Y8, Y9, Y10, Y11, Y12, Y13, Y14, Y15);
10 endmodule

```

## SIMULATION

***(This part is optional depending on the requirement of the lab task)***

*Describe how you build the test bench and do the simulation.*

- *Using Verilog (provide the Verilog code)*

```

module decoder_76138_tb();
    reg A, B, C, G1, G2a, G2b;
    wire Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7;
    decoder_74138 s(A, B, C, G1, G2a, G2b, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
    initial begin
        {G1, G2a, G2b}=3'b011;
        {A, B, C}=3'b000;
        #10 {G1, G2a, G2b}=3'b100;
        repeat(7)
            begin
                #10 {A, B, C}={A, B, C}+1;
            end
        #10
        $finish;
    end
endmodule

```

```


1  `timescale 1ns / 1ps
2  ////////////////////////////////////////////...
21
22
23  module decoder_4_16_tb(
24      );
25      reg A, B, C, G1, G2a, G2b;
26      wire Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7;
27      decoder sim(A, B, C, G1, G2a, G2b, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
28      initial begin
29          {G1, G2a, G2b}=3'b011;
30          {A, B, C}=3'b000;
31          #10 {A, B, C}=3'b100;
32          repeat(7)
33              begin
34                  #10 {A, B, C}={A, B, C}+1;
35              end
36          $finish;
37
38      end
39  endmodule
40

```

- Wave form of simulation result (provide screen shots)

Really sorry that I failed to get the correct result, I asked my classmates and SA but I still cannot solve it. I'll be so happy if I will not

*lose too much mark on this.*

 

- *The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation.*

## CONSTRAINT FILE AND THE TESTING

---

***(This part is optional depending on the requirement of the lab task)***

*Describe how you test your design on the Minisys Practice platform.*

- *Constraint file (provide the screen shots on the feature of a pin and the binding info between pins and the input /output ports)*



```


1  set_property IOSTANDARD LVCMOS33 [get_ports {A}]
2  set_property IOSTANDARD LVCMOS33 [get_ports {B}]
3  set_property IOSTANDARD LVCMOS33 [get_ports {C}]
4  set_property IOSTANDARD LVCMOS33 [get_ports {D}]
5  set_property IOSTANDARD LVCMOS33 [get_ports {Y[0]}]
6  set_property IOSTANDARD LVCMOS33 [get_ports {Y[1]}]
7  set_property IOSTANDARD LVCMOS33 [get_ports {Y[2]}]
8  set_property IOSTANDARD LVCMOS33 [get_ports {Y[3]}]
9  set_property IOSTANDARD LVCMOS33 [get_ports {Y[4]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {Y[5]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {Y[6]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {Y[7]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {Y[8]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {Y[9]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {Y[10]}]
16 set_property IOSTANDARD LVCMOS33 [get_ports {Y[11]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports {Y[12]}]
18 set_property IOSTANDARD LVCMOS33 [get_ports {Y[13]}]
19 set_property IOSTANDARD LVCMOS33 [get_ports {Y[14]}]
20 set_property IOSTANDARD LVCMOS33 [get_ports {Y[15]}]
21
22 set_property PACKAGE_PIN Y9 [get_ports {A}]
23 set_property PACKAGE_PIN W9 [get_ports {B}]
24 set_property PACKAGE_PIN Y7 [get_ports {C}]
25 set_property PACKAGE_PIN Y8 [get_ports {D}]
26
27 set_property PACKAGE_PIN A21 [get_ports {Y0}]
28 set_property PACKAGE_PIN E22 [get_ports {Y1}]
29 set_property PACKAGE_PIN D22 [get_ports {Y2}]
30 set_property PACKAGE_PIN E21 [get_ports {Y3}]
31 set_property PACKAGE_PIN D21 [get_ports {Y4}]
32 set_property PACKAGE_PIN G21 [get_ports {Y5}]
33 set_property PACKAGE_PIN G22 [get_ports {Y6}]
34 set_property PACKAGE_PIN F21 [get_ports {Y7}]
35 set_property PACKAGE_PIN J17 [get_ports {Y8}]
36 set_property PACKAGE_PIN L14 [get_ports {Y9}]
37 set_property PACKAGE_PIN L15 [get_ports {Y10}]
38 set_property PACKAGE_PIN L16 [get_ports {Y11}]
39 set_property PACKAGE_PIN K16 [get_ports {Y12}]
40 set_property PACKAGE_PIN M15 [get_ports {Y13}]
41 set_property PACKAGE_PIN M16 [get_ports {Y14}]
42 set_property PACKAGE_PIN M17 [get_ports {Y15}]

```

•




 - The testing result (provide the screen shots (at least 3 testing scene) to show state of inputs and outputs along with the related descriptions.



- 0000, default, the first is on



 

## THE DESCRIPTION OF OPERATION

---

***(This part is always REQUIRED unless you can get full marks for this lab task)***

*Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.*

- *Problems and solutions*
- *I don't have enough knowledge for decoder and I failed to design the testbench when I was doing this experiment.*
- *I studied combinational logic and asked my friends for help, and they gave me ideas.*

## PART 2: DIGITAL DESIGN LAB (TASK2)

### DESIGN

---

*Describe the design of your system by providing the following information:*



```

1  `timescale 1ns / 1ps
2  ////////////////////////////////////////////...
21
22  module mux74151(EN, S2, S1, S0, D7, D6, D5, D4, D3, D2, D1, D0, Y, W);
23      input EN, S2, S1, S0;
24      input D7, D6, D5, D4, D3, D2, D1, D0;
25      output reg Y; output W;
26      always @* begin
27          if(~EN)
28              case({S2, S1, S0})
29                  3'b000: Y = D0;
30                  3'b001: Y = D1;
31                  3'b010: Y = D2;
32                  3'b011: Y = D3;
33                  3'b100: Y = D4;
34                  3'b101: Y = D5;
35                  3'b110: Y = D6;
36                  3'b111: Y = D7;
37              endcase
38          else
39              Y = 1'b0;
40          end
41          assign W=~Y;
42      endmodule
43

```

```

1  `timescale 1ns / 1ps
2  ////////////////////////////////////////////
3  // Company:
4  // Engineer:
5  //
6  // Create Date: 12/15/2021 09:25:53 PM
7  // Design Name:
8  // Module Name: func_df
9  // Project Name:
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ////////////////////////////////////////////
21
22 module func_df(input A, B,C,D, output Y);
23     assign Y = ~A & ~B & ~C & ~D | B & D | A & C | ~B & C & ~D | ~A & ~B & ~D;
24 endmodule
25

```

```

1  `timescale 1ns / 1ps
2  ////////////////////////////////////////////...
21
22  module mux74151(EN, S2, S1, S0, D7, D6, D5, D4, D3, D2, D1, D0, Y, W);
23      input EN, S2, S1, S0;
24      input D7, D6, D5, D4, D3, D2, D1, D0;
25      output reg Y; output W;
26      always @* begin
27          if(~EN)
28              case({S2, S1, S0})
29                  3'b000: Y = D0;
30                  3'b001: Y = D1;
31                  3'b010: Y = D2;
32                  3'b011: Y = D3;
33                  3'b100: Y = D4;
34                  3'b101: Y = D5;
35                  3'b110: Y = D6;
36                  3'b111: Y = D7;
37              endcase
38          else
39              Y = 1'b0;
40          end
41          assign W=~Y;
42      endmodule
43
44

```

```

1  `timescale 1ns / 1ps
2  ////////////////////////////////////////////...
21
22  module func_1mux(input EN, input S3, S2, S1, S0, output Y, W);
23      reg D7, D6, D5, D4, D3, D2, D1, D0;
24      always @(*)
25      begin
26          D7 = 1; D6 = S0; D5 = 1; D4 = 0; D3 = S0; D2 = S0; D1 = ~S0; D0 = ~S0;
27      end
28      mux74151 mux(EN,S3,S2,S1,D7, D6, D5, D4, D3, D2, D1, D0, Y, W);
29  endmodule
30

```

```

1  `timescale 1ns / 1ps
2  //////////////////////////////////////////////////|..
21
22  module func_2mux(EN, S3, S2, S1, S0, Y);
23      input EN, S3, S2, S1, S0;
24      reg [15:0] D;
25      output reg Y;
26      wire Y1, Y2;
27      wire W;
28      mux74151 m1(EN, S2, S1, S0, D[7], D[6], D[5], D[4], D[3], D[2], D[1], D[0], Y1);
29      mux74151 m2(EN, S2, S1, S0, D[15], D[14], D[13], D[12], D[11], D[10], D[9], D[8], Y2);
30      always @(*)
31          begin D = 16'b1110_1100_1010_0101;
32              case (S3) 0: Y = Y1; 1: Y = Y2;
33              endcase
34          end
35      endmodule
36  ..

```

## SIMULATION

*Describe how you build the test bench and do the simulation.*

- *Using Verilog (provide the Verilog code)*

```

1  `timescale 1ns / 1ps
2
3  module mux74151_tb(
4
5  );
6  reg D0, D1, D2, D3, D4, D5, D6, D7, S0, S1, S2, EN;
7  wire Y;
8  wire Y_reverse;
9  mux74151 u(D0, D1, D2, D3, D4, D5, D6, D7, S0, S1, S2, EN);
10 initial
11     begin
12         {EN, D0, D1, D2, D3, D4, D5, D6, D7} = 9'b11111111;
13         {S2, S1, S0} = 3'b000;
14         EN = 0;
15         #5 {S2, S1, S0} = 3'b000; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00000001;
16         #5 {S2, S1, S0} = 3'b001; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00000010;
17         #5 {S2, S1, S0} = 3'b010; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00000100;
18         #5 {S2, S1, S0} = 3'b011; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00001000;
19         #5 {S2, S1, S0} = 3'b100; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00010000;
20         #5 {S2, S1, S0} = 3'b101; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b00100000;
21         #5 {S2, S1, S0} = 3'b110; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b01000000;
22         #5 {S2, S1, S0} = 3'b111; {D7, D6, D5, D4, D3, D2, D1, D0} = 8'b10000000;
23         #10
24         $finish;
25     end
26 endmodule
27

```


```

1  `timescale 1ns / 1ps
2
3  module func_tb(
4
5  );
6  reg A, B, C, D;
7  wire F_df;
8  func_df x1(A, B, C, D, F_df);
9
10 initial
11     begin
12         {A, B, C, D} = 4'b0000;
13         repeat(15)
14             begin
15                 #10 {A, B, C, D} = {A, B, C, D} + 1;
16             end
17         $finish;
18     end
19 endmodule


```



 - Wave form of simulation result (provide screen shots)
- MUX 74151



 - Func\_tb for dataflow(the other two are the same with data flow)



- The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation
- First, when EN=1, mux is deactivated Then, when EN=0, mux is activated, 8 cases are tested. When {S2,S1,S0}=3'B111, only D7=1, D0~D6=0, {D7,D6,D5,D4,D3,D2,D1,D0} =8'B1000\_0000.The selection works, that it selected the corresponding high level bit in d0~d7.

## THE DESCRIPTION OF OPERATION

*Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.*

- Problems and solutions
- At first I have no idea how to deal with the function with two 74151;
- I asked my classmates and checked the lab slides, and I finally managed to do it.