



DIGITAL DESIGN

ASSIGNMENT REPORT

ASSIGNMENT ID: 12010423

Student Name: 张嘉浩

Student ID: 12010423

PART 1: DIGITAL DESIGN THEORY

Provide your answers here:

12010423 Assignment 4.

JK Flip-flop:

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

Equation

$$Q(t+1) = JQ' + K'Q$$

T Flip-flop:

T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

Equation

$$Q(t+1) = T \oplus Q = TQ' + T'Q$$

2. (a) $A(t+1) = JAQ' + KA'Q = A(t+1) = JAA' + KA'A = 0 + B'A = B'A$
 $A(t+1) = JAQ' + KA'Q = 0 + B'A = B'A$
 $B(t+1) = JBQ' + KBQ = AB' + AB = A(B' + B) = A$
 $B(t+1) = JBQ' + KBQ = AB' + AB = A$

(b) State Diagram:

```

graph TD
    00((00)) -- 0 --> 00
    00 -- 1 --> 01((01))
    01 -- 0 --> 00
    01 -- 1 --> 11((11))
    11 -- 0 --> 01
    11 -- 1 --> 10((10))
    10 -- 0 --> 00
    10 -- 1 --> 01
  
```

Binary repeated sequence: 0, 4, 6, 7, 3, 1.

We need 3 bits, 3 flip-flops.

① State Table.

Present State			Next State			Flip-Flop Inputs		
$C(t)$	$B(t)$	$A(t)$	$C(t+1)$	$B(t+1)$	$A(t+1)$	TC	TB	TA
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	1
0	1	0	X	X	X	X	X	X
0	1	1	0	0	1	0	1	0
1	0	0	1	1	0	0	1	0
1	0	1	X	X	X	X	X	X
1	1	0	1	1	1	0	0	1
1	1	1	0	1	1	1	0	0

② Input equation

$TQ_0:$

② Input Equations

TC_0 :

$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	1	0	X
1	0	X	0	1

$$TC_0 = C_1' C_0 + C_1 C_0' = C_0 \oplus C_1$$

TC_1 :

$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	0	1	X
1	1	X	0	0

$$TC_1 = C_1' C_2 + C_1 C_2' = C_1 \oplus C_2$$

TC_2 :


$C_2 \backslash C_1 C_0$	00	01	11	10
0	1	0	0	X
1	0	X	1	0

$$TC_2 = C_0 C_2 + C_0' C_2' = (C_0 \oplus C_2)'$$


④ State Diagram

④

③ Circuit Diagram

 

④ State diagram before connection.

 


OO nova 7 5G
OO AIQUAD CAMERA



计算机科学与工程系
Department of Computer Science and Engineering

Digital Design Assignment

State Diagram after connection.

 

4. Truth-table for full adder.

Inputs			Outputs	
x	y	Q	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

"one flip-flop &
two inputs x and y
one output s"

D flip-flop

D	Q(t+1)
0	0
1	1

$$S = x \oplus y \oplus Q$$


$$C = xQ + xy + yQ$$

$$D = C = xQ + xy + yQ = Q(t+1)$$

NOVO 7 5G
AI QUAD CAMERA


State Table :

Inputs				Output
x	y	$Q(t)$	$Q(t+1)$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

5. Shift Register and a D flip-flop.

① State Diagram

 


② State Table

Q	Output	Q _{t+1}	Input	D
0	0	0	0	0
0	1	1	0	1
1	0	1	1	1
1	1	1	0	1

③ Input equation: $D = Q_t + \text{register's output}$

④ Output equation: $Q_{t+1} = D$; register's input = $Q_t \oplus \text{register's output}$

⑤ Circuit Diagram

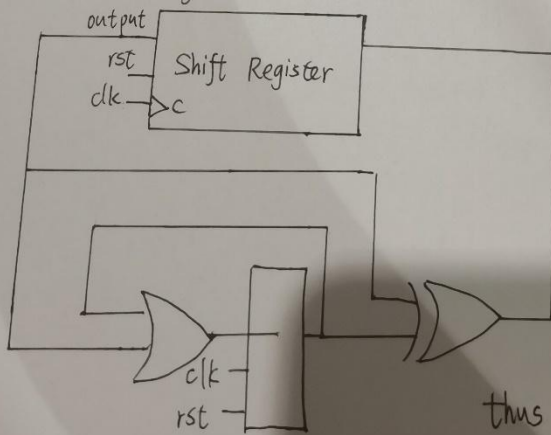

thus we finished the design of the circuit diagram

PART 2: DIGITAL DESIGN LAB (TASK1)

DESIGN

(This part is always REQUIRED)

Describe the design of your system by providing the following information:

- Verilog design (provide the Verilog code)

```

`timescale 1ns / 1ps

module JK_FlipFlop(
    input clk,
    input rst_low,
    input J,
    input K,
    output reg Q
);

    always@(posedge clk, negedge rst_low)
    if(~rst_low) begin
        Q <= 0;
    end
    else begin
        case ({J, K})
            2'b00 : Q = Q;
            2'b01 : Q = 0;
            2'b10 : Q = 1;
            2'b11 : Q = ~Q;
        endcase
    end
endmodule

```

```

1  `timescale 1ns / 1ps
2
3  module circuit(
4      input clk,
5      input rst_low,
6      input x,
7      output A,
8      output B
9  );
10
11     JK_FlipFlop JK1 (.clk(clk), .rst_low(rst_low), .J(~x), .K(B), .Q(A));
12     JK_FlipFlop JK2 (.clk(clk), .rst_low(rst_low), .J(x), .K(~A), .Q(B));
13
14
15 endmodule

```

SIMULATION

(This part is optional depending on the requirement of the lab task)

Describe how you build the test bench and do the simulation.

- Using Verilog (provide the Verilog code)
- JK Flip-Flop simulation src

```
1  `timescale 1ns / 1ps
2
3  module JK_FlipFlop_sim();
4      reg clk = 1;
5      reg rst_low = 0;
6      reg J = 0;
7      reg K = 0;
8      wire Q;
9
10     JK_FlipFlop JKFF (.clk(clk), .rst_low(rst_low), .J(J), .K(K), .Q(Q));
11
12     always
13     #5 clk = ~clk;
```

```
15     initial begin
16         #20
17         rst_low = 1;
18         J <= 0;
19         K <= 0;
20         #20
21         J <= 0;
22         K <= 1;
23         #20
24         J <= 1;
25         K <= 0;
26         #20
27         J <= 1;
28         K <= 1;
29         #20
30         $finish;
31     end
32 endmodule
```

- Circuit simulation src


```

3  module circuit_sim();
4      reg clk = 1;
5      wire A, B;
6      reg x;
7      reg rst_low;
8
9      always
10     #5 clk = ~clk;
11
12     circuit c(.clk(clk), .rst_low(rst_low), .x(x), .A(A), .B(B));
13
14     initial
15     begin
16         rst_low = 0;
17         #10
18         rst_low = 1;
19         x = 0;
20
21         #40
22         x = 1;
23         #40
24         $finish();
25     end
26 endmodule


```

- Wave form of simulation result (provide screen shots)
- JK Flip-Flop simulation

waveform

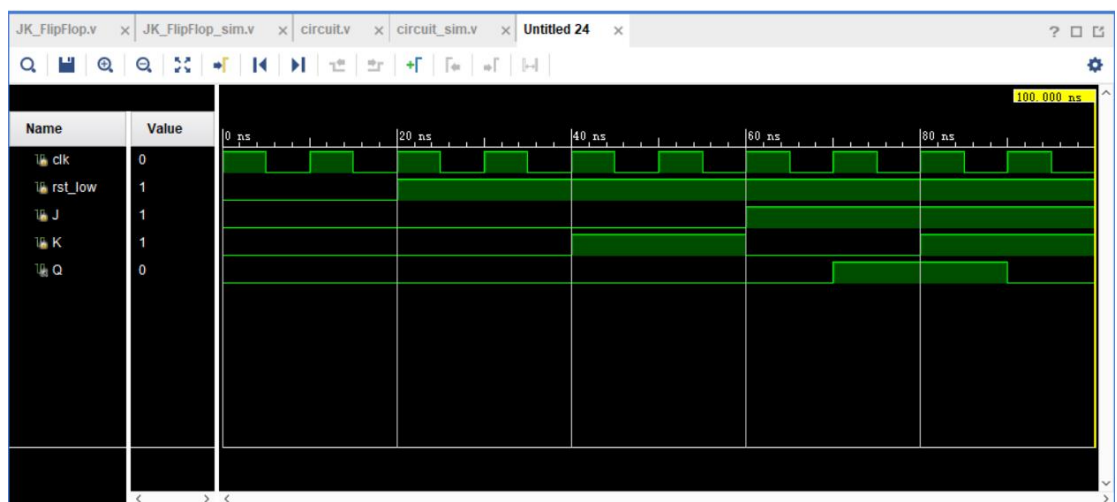

- Circuit simulation waveform

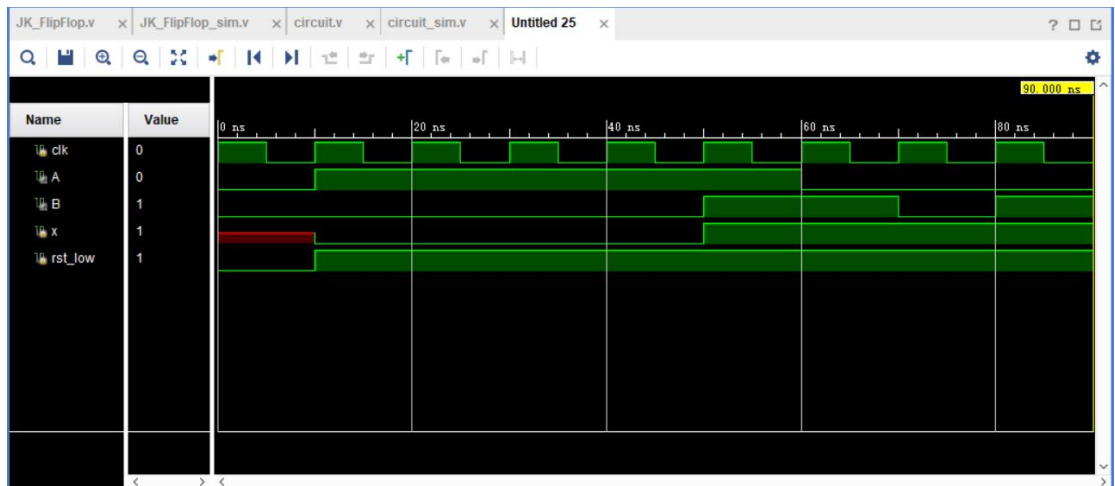

- As far as you can see, the simulation result is exactly the same as it should be.
- As for the JK flip-flop, for instance, when `rst_low` is 1 (at high electrical level), the process is on. When J is 0 and K is 0, we have $Q = 0$. When J is 0 and K is 1, we have $Q = 0$.
- As for the circuit, when `rst_low` is 1, A is 0 and B is 1, we have $x = 0$. When A is 0 and B is 0, we have $x = 1$.

THE DESCRIPTION OF OPERATION

(This part is always REQUIRED unless you can get full marks for this lab task)

Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.

- This is just a simple implementation of the knowledge we've learnt from the JK flipflop in sequential logic. Nevertheless, I still spent plenty of time just to write this simple code. The problem is that I cannot implement the knowledge I learnt into the Verilog code efficiently. I seek for the book and lecture slides for help, and finally managed to do it.

PART 2: DIGITAL DESIGN LAB (TASK2)

DESIGN

- *Shift Register 74195 src*

```
1 module Shift_Register_74195 (  
2     input MR_n, CP, PE_n, J, K_n,  
3     input D3, D2, D1, D0,  
4     output reg Q3, Q2, Q1, Q0,  
5     output Q0_n  
6 );  
7     wire K;  
8     assign Q0_n = ~Q0;  
9     assign K = ~K_n;  
10    always @(posedge CP, negedge MR_n) begin  
11        if(!MR_n)  
12            {Q3, Q2, Q1, Q0} <= 4'b0000;  
13        else  
14            if (!PE_n) begin  
15                {Q3, Q2, Q1, Q0} <= {D3, D2, D1, D0};  
16            end  
17        else  
18            case ({J, K})  
19                2'b00:{Q3, Q2, Q1, Q0} <= {Q2, Q1, Q0, Q0};  
20                2'b01:{Q3, Q2, Q1, Q0} <= {Q2, Q1, Q0, 1'b0};  
21                2'b10:{Q3, Q2, Q1, Q0} <= {Q2, Q1, Q0, 1'b1};  
22                2'b11:{Q3, Q2, Q1, Q0} <= {Q2, Q1, Q0, ~Q0};  
23            endcase  
24        end  
25    endmodule
```

- *Johnson Counter src*

```

3 module Johnson_Counter(input clk,
4                         input rst_n,
5                         output [3:0] out);
6     reg [3:0] D = 0;
7     reg J, K_n;
8     reg PE_n = 1;
9     wire out0_n;
10
11     Shift_Register_74195 SR(.MR_n(rst_n), .CP(clk), .PE_n(PE_n), .J(J), .K_n(K_n),
12                            .D3(D[3]), .D2(D[2]), .D1(D[1]), .D0(D[0]),
13                            .Q3(out[0]), .Q2(out[1]), .Q1(out[2]), .Q0(out[3]), .Q0_n(out0_n));
14
15     always @(out[0]) begin
16         if (~out[0]) begin
17             J = 1'b1;
18             K_n = 1'b1;
19         end
20         else begin
21             J = 1'b0;
22             K_n = 1'b0;
23         end
24     end
25
26 endmodule
27

```

SIMULATION

Describe how you build the test bench and do the simulation.

- Using Verilog (provide the Verilog code)
- *Shift Register 74195 simulation src*


```

1  `timescale 1ns / 1ps
2
3  module Shift_Register_74195_sim();
4      reg clk = 1;
5      reg rst_n;
6      reg PE_n;
7      reg J, K_n;
8      reg[3:0] D;
9      wire[3:0] Q;
10     wire Q0_n;
11
12     Shift_Register_74195 sr(.MR_n(rst_n), .CP(clk), .PE_n(PE_n), .J(J), .K_n(K_n),
13     .D3(D[3]), .D2(D[2]), .D1(D[1]), .D0(D[0]),
14     .Q3(Q[3]), .Q2(Q[2]), .Q1(Q[1]), .Q0(Q[0]), .Q0_n(Q0_n));
15
16     always #10
17     clk = ~clk;
18
19     initial
20     begin
21         rst_n = 0;
22         #80
23         D = 4'b1010;
24         rst_n = 1;
25         PE_n = 0;
26         {J, K_n} = 2'b00;
27         #80
28         PE_n = 1;
29         {J, K_n} = 2'b01;
30         #80
31         {J, K_n} = 2'b00;
32         #80
33         {J, K_n} = 2'b11;
34         #80
35         {J, K_n} = 2'b10;
36         #40
37         $finish();
38     end
39 endmodule
40

```


- Johnson Counter simulation src

```


1  `timescale 1ns / 1ps
2
3  module Johnson_Counter_sim();
4      reg clk = 1;
5      reg rst_n = 0;
6      wire[3:0] out;
7
8      Johnson_Counter JC(.clk(clk), .rst_n(rst_n), .out(out));
9
10     always
11     #10 clk = ~clk;
12
13     initial
14     begin
15         #10
16         rst_n = 1;
17         #200
18         $finish();
19     end
20
21 endmodule

```

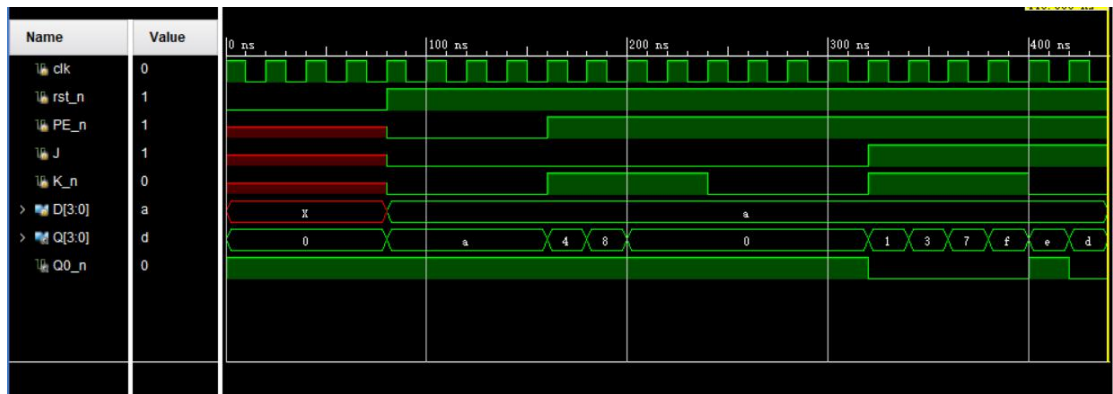-
- Wave form of simulation result (provide screen shots)
- Shift Register 74195 simulation waveform



- Johnson Counter simulation waveform

 

- *As far as you can see, the waveform result is exactly the same as it theoretically should be.*
- *For instance, as for the shift register 74195, when rst_n is 1, PE_n is 1, J is 1 and K_n is 0. We have D = a, Q = d.*
- *As for the Johnson Counter, when rst_n is 1, the output c changes from 0 to 8, c, e, f, 7, 3, 1 and 0 again as a circulation, as the simulation time goes.*

THE DESCRIPTION OF OPERATION

Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.

- *The main problem is that I'm not quite familiar with this part of knowledge. Thanks to the code in lab13, otherwise I'll spent much more time figuring out how to write shift register 74195 and Johnson Counter code. I should review the lecture slides Prof. G use in class and refer to the textbook more often.*

PART 2: DIGITAL DESIGN LAB (TASK3)

DESIGN

Describe the design of your system by providing the following information:

Top module

```

1 module top(
2     input clk,
3     input rst,
4     input switch,
5     output [7:0] seg_en,
6     output [7:0] seg_out
7 );
8     wire [2:0] scan_cnt;
9     freq_div fd(.clk(clk), .rst(rst), .scan_cnt(scan_cnt));
10    segtube st(.clk(clk), .scan_cnt(scan_cnt), .rst(rst), .switch(switch), .seg_en(seg_en), .seg_out(seg_out));
11
12 endmodule

```

Frequency divider module

```

1 module freq_div(
2     input clk,
3     input rst,
4     output reg [2:0] scan_cnt
5 );
6
7     reg clk_seg;
8     reg [19:0] cnt;
9
10    parameter period = 250000; //400Hz
11
12    always @(posedge clk, posedge rst) //分频为clk_seg
13    begin
14        if (rst) //复位
15        begin
16            cnt <= 0; //cnt归0
17            clk_seg <= 0; //clk归0
18        end
19        else begin
20            if (cnt == (period >> 1) - 1) //右移除以2为半个周期, 当半个周期结束
21            begin
22                clk_seg <= ~clk_seg; //clk取反, 两次取反为一个周期
23                cnt <= 0; //cnt归0
24            end
25            else
26                cnt <= cnt + 1; //cnt递增
27        end
28    end

```

```

30 always@(posedge clk_seg, posedge rst) //根据clk_seg改变scan_cnt
31 begin
32     if (rst) //复位
33         scan_cnt <= 0; //scan_cnt归0
34     else begin
35         scan_cnt <= scan_cnt + 1; //scan_cnt递增
36         if (scan_cnt == 3'd7) //scan_cnt一个周期完成
37             scan_cnt <= 0; //scan_cnt归0
38     end
39 end
40 endmodule

```

7-segtube module

```

1  `timescale 1ns / 1ps
2
3  module segtube(
4      input clk,
5      input [2:0] scan_cnt,
6      input rst,
7      input switch,
8      output reg [7:0] seg_en,
9      output reg [7:0] seg_out
10 );
11
12 always @(scan_cnt) begin
13     case(scan_cnt)
14         0: seg_en = 8'b0111_1111;
15         1: seg_en = 8'b1011_1111;
16         2: seg_en = 8'b1101_1111;
17         3: seg_en = 8'b1110_1111;
18         4: seg_en = 8'b1111_0111;
19         5: seg_en = 8'b1111_1111;
20         6: seg_en = 8'b1111_1111;
21         7: seg_en = 8'b1111_1111;
22         default: seg_en = 8'b1111_1111;
23     endcase
24 end
25

```

```

26  always @(scan_cnt) begin
27      if(switch) begin
28          case(scan_cnt)
29              0 : seg_out <= 8'b10100100;
30              1 : seg_out <= 8'b11000000;
31              2 : seg_out <= 8'b10100100;
32              3 : seg_out <= 8'b11111001;
33              4 : seg_out <= 8'b10001110;
34              default: seg_out <= 8'b11111111;
35          endcase
36      end
37      else begin
38          case(scan_cnt)
39              0 : seg_out <= 8'b11000110;
40              1 : seg_out <= 8'b10010010;
41              2 : seg_out <= 8'b10100100;
42              3 : seg_out <= 8'b11000000;
43              4 : seg_out <= 8'b11111000;
44              default: seg_out <= 8'b11111111;
45          endcase
46      end
47  end
48  endmodule

```

CONSTRAINT FILE AND THE TESTING

- *Constraint File xdc*


```

1  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[7]}]
2  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[6]}]
3  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[5]}]
4  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[4]}]
5  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[3]}]
6  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[2]}]
7  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[1]}]
8  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[0]}]
9  set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[7]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[6]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[5]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[4]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[3]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[2]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[1]}]
16 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[0]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports {clk}]
18 set_property IOSTANDARD LVCMOS33 [get_ports {rst}]
19 set_property IOSTANDARD LVCMOS33 [get_ports {switch}]
20

```

```

21 set_property PACKAGE_PIN C19 [get_ports {seg_en[0]}]
22 set_property PACKAGE_PIN E19 [get_ports {seg_en[1]}]
23 set_property PACKAGE_PIN D19 [get_ports {seg_en[2]}]
24 set_property PACKAGE_PIN F18 [get_ports {seg_en[3]}]
25 set_property PACKAGE_PIN E18 [get_ports {seg_en[4]}]
26 set_property PACKAGE_PIN B20 [get_ports {seg_en[5]}]
27 set_property PACKAGE_PIN A20 [get_ports {seg_en[6]}]
28 set_property PACKAGE_PIN A18 [get_ports {seg_en[7]}]
29
30 set_property PACKAGE_PIN F15 [get_ports {seg_out[0]}]
31 set_property PACKAGE_PIN F13 [get_ports {seg_out[1]}]
32 set_property PACKAGE_PIN F14 [get_ports {seg_out[2]}]
33 set_property PACKAGE_PIN F16 [get_ports {seg_out[3]}]
34 set_property PACKAGE_PIN E17 [get_ports {seg_out[4]}]
35 set_property PACKAGE_PIN C14 [get_ports {seg_out[5]}]
36 set_property PACKAGE_PIN C15 [get_ports {seg_out[6]}]
37 set_property PACKAGE_PIN E13 [get_ports {seg_out[7]}]
38
39 set_property PACKAGE_PIN Y18 [get_ports {clk}]
40 set_property PACKAGE_PIN P20 [get_ports {rst}]
41 set_property PACKAGE_PIN W4 [get_ports {switch}]
42

```





THE DESCRIPTION OF OPERATION

Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.

- In charge of the 7seg tube display section in my digital design project, I complete this task without much difficulty. The challenge for me is modular programming. I write the display of 7seg tube all in one module, without separating the frequency divider and display part. Modular programming is absolutely a nice habit and an important programming thought that I must be skilled.*